
 


 

# VHDL CODE FOR HALF AND FULL SUBTRACTOR



Half-Subtractor Circuit





<i>1<sup>st</sup> Bit or Digit</i>	<i>2<sup>nd</sup> Bit or Digit</i>	<i>Difference</i>	<i>Borrow</i>
0	0	0	0
1	0	1	0
0	1	1	1
1	1	0	0

## VHDL code for Half Subtractor:

```
library IEEE;
use IEEE.std_logic_1164.all;
entity half_sub is
port(A,B: in std_logic;
diff,borrow : out std_logic
);
end half_sub;
architecture flow of half_sub is
begin
diff<= A xor B;
borrow<=not(A) and B;
end flow;
```

# TRUTH TABLE OF FULL SUBTRACTOR

INPUT			OUTPUT	
A	B	Bin	D	Bout
0	0	0	0	0
0	0	1	1	1
0	1	0	1	1
0	1	1	0	1
1	0	0	1	0
1	0	1	0	0
1	1	0	0	0
1	1	1	1	1





		B Bin			
		00	01	11	10
A	0	0	1	0	1
	1	1	0	1	0


$$D = A'B'Bin + AB'Bin' + A'BBin' + ABBin$$

		B Bin			
		00	01	11	10
A	0	0	1	1	1
	1	0	0	1	0

 
$$\text{Bout} = A' \text{Bin} + A' B + B \text{Bin}$$





 


# Full Subtractor

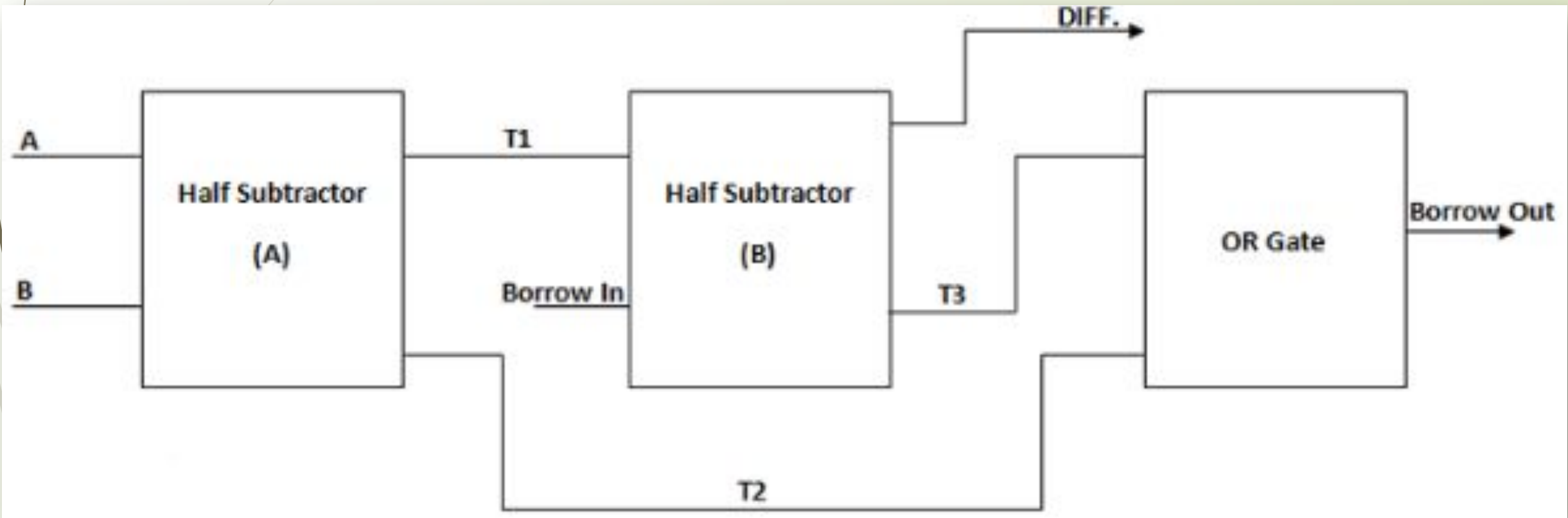



```
library IEEE;
use IEEE.std_logic_1164.all;

entity full_sub is
    port(A,B,borrow_in: in std_logic;
         diff,borrow_out : out std_logic
    );
end full_sub;

architecture flow of full_sub is
    component half_sub is
        port(A,B : in std_logic;
             diff,borrow : out std_logic
        );
    end component;

    component or_gate is
        port(A,B : in std_logic;
             Y : out std_logic
        );
    end component ;

    signal T1,T2,T3:std_logic;

    begin

    half_sub1: half_sub port map (A=>A,B=>B,diff=>T1,borrow=>T2);
    half_sub2: half_sub port map(A=>T1,B=>borrow_in,diff=>diff,borrow=>T3);
    or_gate1: or_gate port map(A=>T3,B=>T2,Y=>borrow_out);

    end flow;
```