

Code For 4x1 Multiplexer

```
Library ieee;
use ieee.std_logic_1164.all;

entity mux_41 is
port( signal data :in std_logic_vector(3 downto 0);
      signal select_line: in std_logic_vector(1 downto 0);
      signal enable: in std_logic;
      signal output:out std_logic );
end mux_41;

architecture sim of mux_41 is
begin
output<= data(3) when select_line="00" and enable='1' else
data(2) when select_line="01" and enable='1' else
data(1) when select_line="10" and enable='1' else
data(0) when select_line="11" and enable='1' else
'X';
end sim;
```